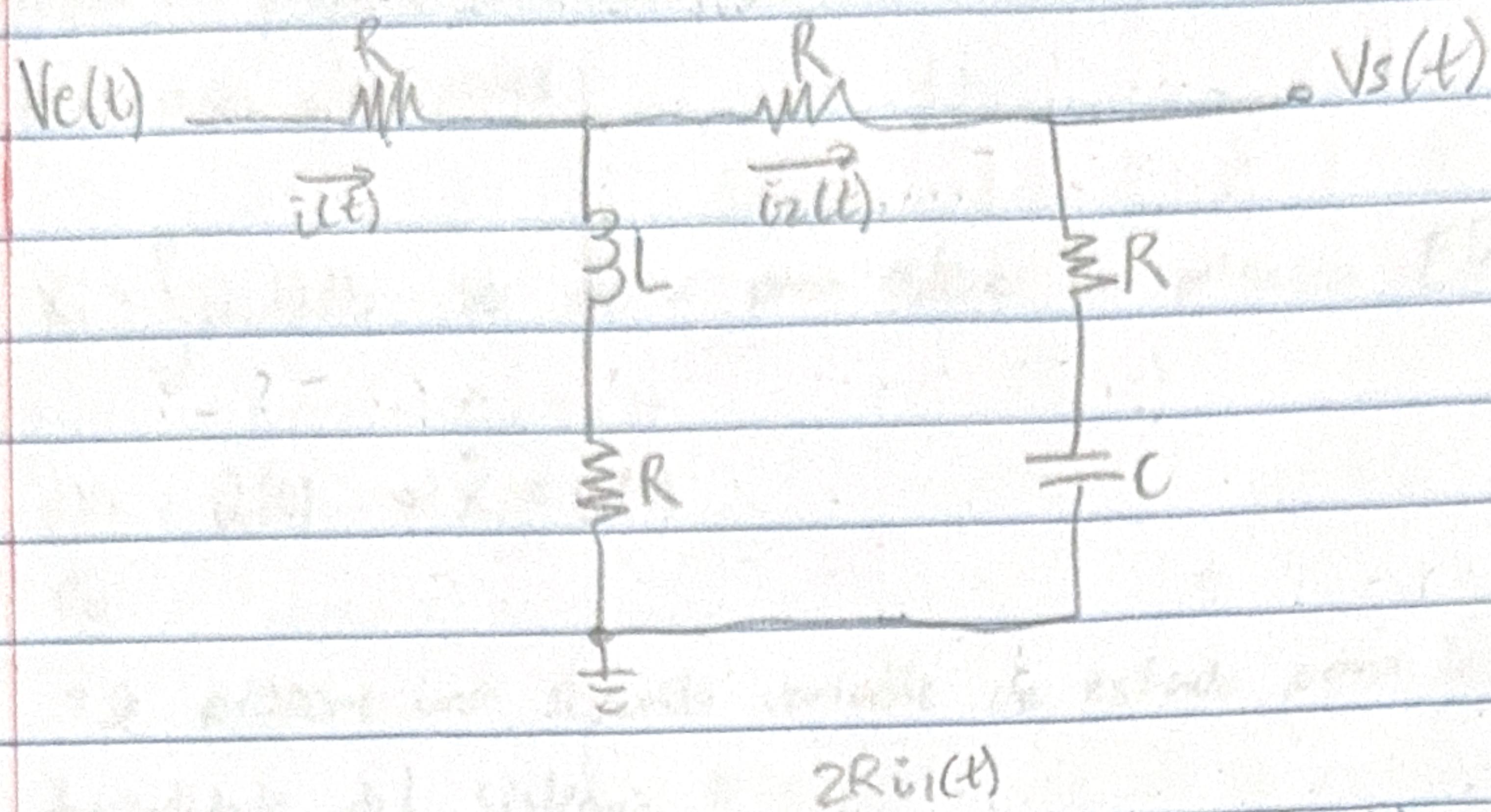


Práctica 1



- Ecuaciones principales

$$V_e(t) = \underline{R i_1(t)} + L \frac{d[i_1(t) - i_2(t)]}{dt} + R \underline{i_1(t) - i_2(t)}$$

$$L \frac{d[i_1(t) - i_2(t)]}{dt} + R \underline{i_1(t) - i_2(t)} = \underline{R i_2(t)} + R i_2(t) + \frac{1}{C} \int i_2(t) dt$$

$$V_s(t) = \underline{R i_2(t)} + \frac{1}{C} \int i_2(t) dt$$

- Modelo de ecuaciones integro-diferenciales

$$i_1(t) = \left[V_e(t) - L \frac{d[i_1(t) - i_2(t)]}{dt} + R i_2(t) \right] \frac{1}{Z_R}$$

$$i_2(t) = \left[L \frac{d[i_1(t) - i_2(t)]}{dt} + R i_1(t) - \frac{1}{C} \int i_2(t) dt \right] \frac{1}{Z_R}$$


$$V_s(t) = \underline{R i_2(t)} + \frac{1}{C} \int i_2(t) dt$$

$$R = 3.3 \text{ k}\Omega$$

$$C = 4.7 \times 10^{-6} \text{ F}$$

$$L = 3.3 \times 10^{-3} \text{ H}$$

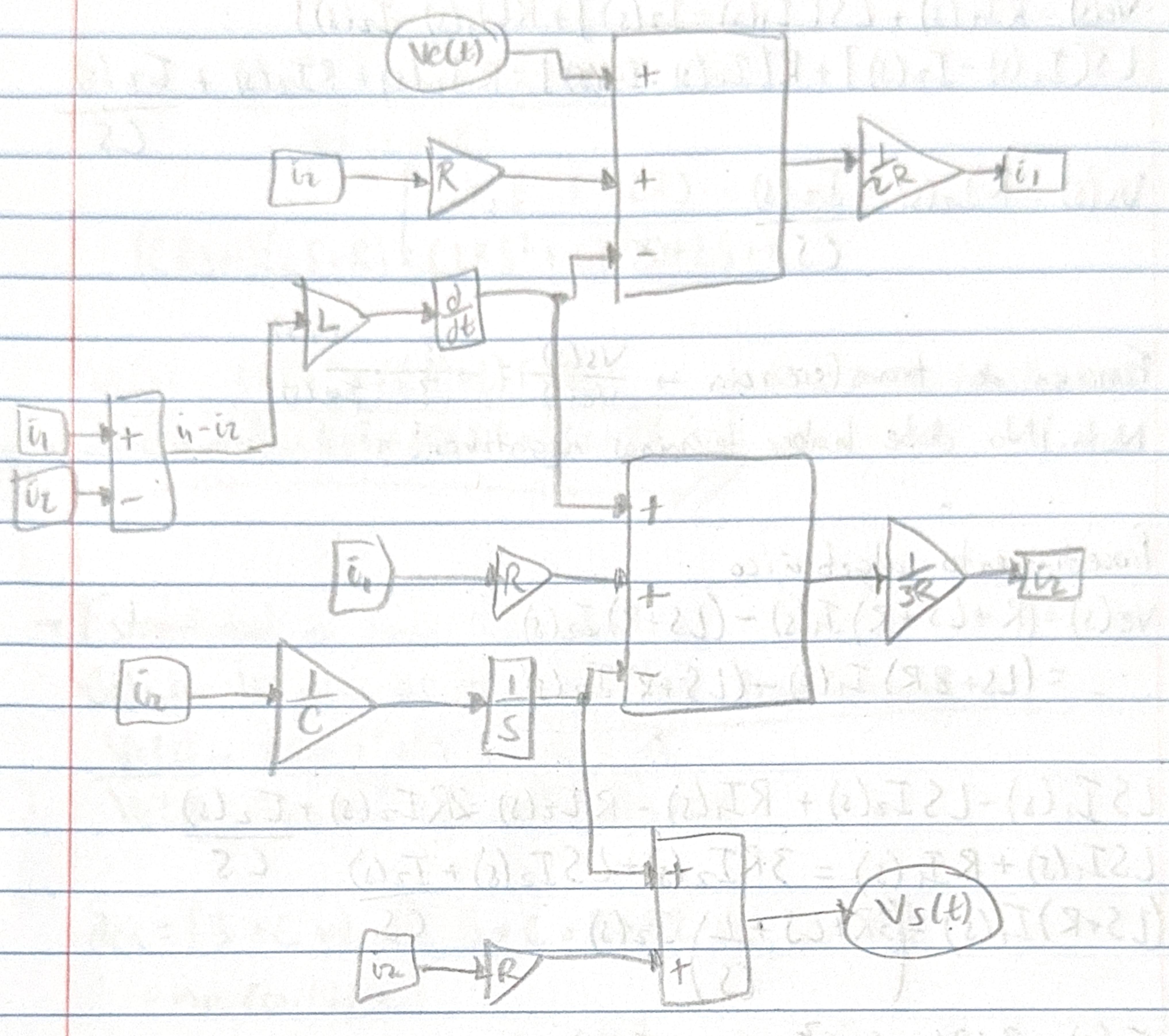En simulink con Goto y From para ir e ir de circuito



$$(1) \quad 1 + \frac{1}{(R+2s)} + \frac{1}{(R+2s)^2} = \frac{1}{(R+2s)}$$

$$(1) \quad 1 + \frac{1}{(R+2s)} + \frac{1}{(R+2s)^2} = \frac{1}{(R+2s)}$$

$$(1) \quad 1 + \frac{1}{(R+2s)} + \frac{1}{(R+2s)^2} = \frac{1}{(R+2s)}$$

$$1 + \frac{1}{(R+2s)} + \frac{1}{(R+2s)^2} = \frac{1}{(R+2s)}$$

función de transferencia

Transformada de Laplace

$$V_e(s) = RI_1(s) + LS[I_1(s) - I_2(s)] + R[I_1(s) - I_2(s)]$$

$$LS[I_1(s) - I_2(s)] + R[I_1(s) - I_2(s)] = R\bar{I}_2(s) + RI_2(s) + \frac{I_2(s)}{CS}$$

$$V_s(s) = RI_2(s) + \frac{I_2(s)}{CS} = \frac{(RS+1)}{CS} I_2(s)$$

$$\text{Función de transferencia} \rightarrow \frac{V_s(s)}{V_e(s)} = \frac{?}{?} \xrightarrow{?} \frac{I_2(s)}{I_2(s)}$$

Nota: ¡No debe haber términos negativos! sería inestable y no se quiere eso

Procedimiento algebraico

$$\begin{aligned} V_e(s) &= (R + LS + R) I_1(s) - (LS + R) I_2(s) \\ &= (LS + 2R) I_1(s) - (LS + R) I_2(s) \quad \text{ec. 2} \end{aligned}$$

$$LSI_1(s) - LSI_2(s) + RI_1(s) - RI_2(s) = 2RI_2(s) + I_2(s)$$

$$LSI_1(s) + RI_1(s) = 3RI_2(s) + LSI_2(s) + \frac{I_2(s)}{CS}$$

$$(LS + R) I_1(s) = \left(3R + LS + \frac{1}{CS}\right) I_2(s)$$

$$\begin{aligned} I_1(s) &= \frac{3(RS + CLS^2 + 1)}{CS(LS + R)} I_2(s) \\ &= \frac{CLS^2 + 3(RS + 1)}{CS(LS + R)} I_2(s) \quad \text{ec. 3} \end{aligned}$$

- Sustituir $I_1(s)$ en ec. 2.

$$V_e(s) = (LS + 2R) \left(\frac{CLS^2 + 3(RS + 1)}{CS(LS + R)} I_2(s) \right) - (LS + R) I_2(s)$$

$$= \left[\frac{(LS + 2R)(CLS^2 + 3(RS + 1)) - CS(LS + R)(LS + R)}{CS(LS + R)} \right] I_2(s)$$

$$\cancel{CLS^3 + 3CLRS^2 + LS + 2CLR^2S^2 + 6CR^2S + 2R} - \cancel{CLS^3 - 2CLRS^2 - CR^2S}$$

$$V_e(s) = \frac{3CLRS^2 + (5CR^2 + L)S + 2R}{CS(LS + R)} I_2(s)$$

$$\underline{V_s(s) \frac{CRs+1}{Cs} I_2(s)}$$

$$\underline{\frac{3CLRS^2 + (SCR^2 + L)s + 2R}{Cs(Ls + R)} I_2(s)}$$

$$(CRs+1)(Ls+R) = CLRS^2 + CR^2s + LS + R$$

$$\underline{\frac{V_s(s)}{V_e(s)} = \frac{CLRS^2 + (CR^2 + L)s + R}{3CLRS^2 + (5CR^2 + L)s + 2R}}$$

Funció de transferencia

- Estabilidad en lazo abierto

• Calcular los polos de la función de transferencia

$$V_s(s) = CLRS^2 + (CR^2 + L)s + R$$


$$V_e(s) = 3CLRS^2 + (5CR^2 + L)s + 2R$$

$$\text{den} = [3 * C * L * R, 5 * C * R + 2 + L, 2 * R]$$

$$L = \text{np.roots}(\text{den})$$

fprint: Las raíces son $\{L[0]\}$ y $\{L[1]\}$

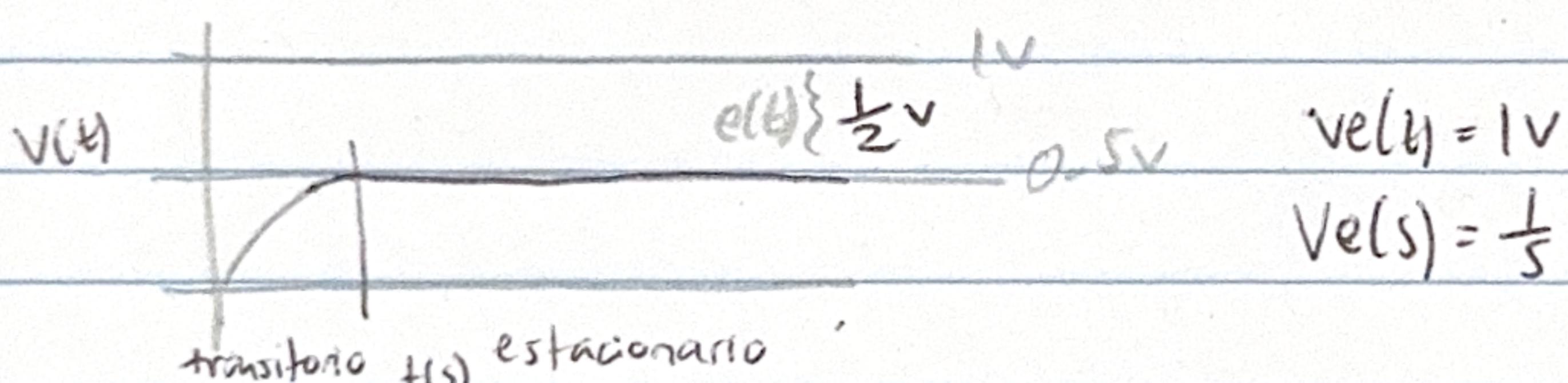El sistema presenta una respuesta estable y sobreamortiguada.



Errores en estado estacionario

$$e(s) = \lim_{s \rightarrow 0} sV_e(s) \left[1 - \frac{V_s(s)}{V_e(s)} \right]$$

$$= \lim_{s \rightarrow 0} s \cdot \frac{1}{s} \left[1 - \frac{CLRS^2 + (CR^2 + L)s + R}{3CLRS^2 + (5CR^2 + L)s + 2R} \right]$$

$$= \frac{R}{2R} \quad e(t) = \frac{1}{2}V$$